

Digital Circuits and VHDL – Overview and Examples

Florian Hagemann

Abstract—Here be an abstract...

CONTENTS

I	Introduction	1
II	Digital Circuits	1
II-A	Electronic Switches: Transistors	2
II-B	Boolean Algebra	2
III	Introduction to VHDL	2
III-A	Hardware Description Languages	2
III-B	Basic Syntax	2
III-C	Blackbox Diagrams and Entities	2
IV	Combinational Circuits	2
IV-A	Basic Logic Gates	2
V	Sequential Circuits	2
VI	Finite State Machines (FSM)	2
VI-A	Moore Machines	2
VI-B	Mealy Machines	2
References		2

I. INTRODUCTION

II. DIGITAL CIRCUITS

WHAT is a *digital circuit*? To understand this, we need to examine each word separately. A *circuit* is a closed loop that allows electricity to flow. Typically it consists of a power source and some device (e.g., a motor, LED, etc.) that uses that electricity. A circuit needs to be closed in order for the electricity to flow through it [1]. *Digital* comes from the Latin “*digitalis*” meaning finger or toe. Digital can mean “something to do with digits (fingers or toes)” but can also mean the “property of representing values as discrete, often binary, numbers rather than a continuous spectrum” [2].

A **digital circuit** is a closed loop that electricity can flow through that uses discrete values. Most often these values are ‘1’ (on, high, or true) and ‘0’ (off, low, or false)¹. This system of using two values is called *binary*.

We can now look at a very basic example (Fig. 1) of what we can do by defining binary values. When the switch is closed, electricity can flow through the LED and it will light up; if it is not closed, no electricity will flow.

Thanks to ...

¹You can use more than two values but binary is most common. See https://en.wikipedia.org/wiki/Ternary_computer

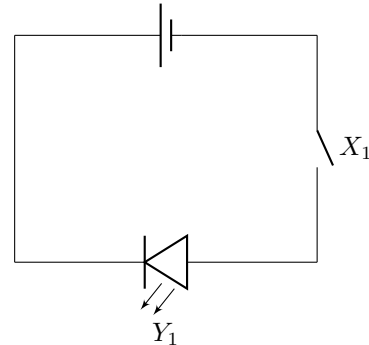


Fig. 1. Simple series circuit with a voltage source, switch, and LED.

We only care for the switch and the output state of the circuit though, not what the power source is or what the output is connected to, so we can simplify our diagram (Fig. 2).

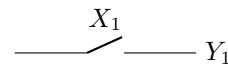


Fig. 2. Simplified diagram of Fig. 1.

So we know if we press X_1 , Y_1 will be set high or to ‘1’. We can illustrate this using a *truth table* (Tab. I):

TABLE I
TRUTH TABLE FOR FIG. 2

X_1	Y_1
0	0
1	1

With a truth table we can read what our output will be for any input. At this point in time this is overkill, but it gets more useful the more switches we add. For example, we can add another switch in series (Fig. 3).

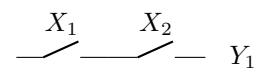


Fig. 3. Two switches in series

Now if none or only one switch is turned on, the output will stay low. But if both switches are turned on, the output will be high. So we can check a condition just using switches and electricity. But we might also notice that if we want to do something more complex, we will need more and more switches which we have to flip manually.

TABLE II
TRUTH TABLE FOR FIG. 3

X_1	X_2	Y_1
0	0	0
1	0	0
0	1	0
1	1	1

A. Electronic Switches: Transistors

Luckily there is an invention that solves the issue of us having to flip switches by hand. The **transistor** is a semiconductor device used (among other uses) to switch electrical signals². Transistors usually have three terminals a *source* (or *collector*), *gate* (or *base*), and *drain* (or *emitter*). You might have heard a water analogy used to explain electricity before and we can use it again to understand the transistor. The water flow comes from the source, applying a voltage to the gate opens it, and the water drains through the drain. If we don't open the gate, no water can flow and the drain will be dry. There are many types of transistors, but we can't talk about all of them, but in general they do the same thing.

We can now replace our switches in Figure 3 with transistors, we will look at the circuit as a whole though (Fig. 4). Now we only need to apply a voltage to X_1 and X_2 instead of switching them. While at this scale it will still be the same amount of work for us to switch the voltages, the advantage of this design is that we can now plug the output of these transistors into another transistor to switch that automatically.

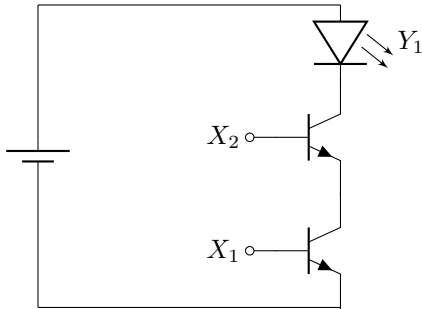


Fig. 4. Simple transistor switch circuit controlling an LED output (Y_1) via input signals X_1 and X_2 .

We represent transistors (here NPN-Transistors) using this symbol (Fig 5).

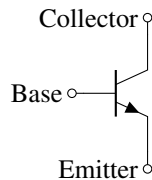


Fig. 5. NPN-Transistor

²We will not talk about how a transistor works. See <https://en.wikipedia.org/wiki/Transistor> or search the web for more information.

B. Boolean Algebra

We've been treating the binary system mostly as "on" and "off" up to this point, but in the beginning we also defined '0' as *false* and '1' as *true*. We can use mathematical formula to describe our circuits. For example we can describe the circuit in Figure 3 with the formula

$$X_1 \wedge X_2 = Y_1$$

. The $\wedge$ symbol means logical AND with the upside down $\vee$ meaning logical OR. How they operate is in the name:

- For $\wedge$ (AND): *Input One and Input Two* need to be true for the output to be true.
- For $\vee$ (OR): *Input One or Input Two* needs to be true for the output to be true.

We can also look at the truth tables of both logical operations (remember that we represent *false* with 0 and *true* with 1):

TABLE III
TRUTH TABLES FOR AND AND OR OPERATIONS

AND ($X_1 \wedge X_2$)			OR ($X_1 \vee X_2$)		
X_1	X_2	Y_1	X_1	X_2	Y_1
0	0	0	0	0	0
1	0	0	1	0	1
0	1	0	0	1	1
1	1	1	1	1	1

III. INTRODUCTION TO VHDL

A. Hardware Description Languages

B. Basic Syntax

C. Blackbox Diagrams and Entities

IV. COMBINATIONAL CIRCUITS

A. Basic Logic Gates

V. SEQUENTIAL CIRCUITS

VI. FINITE STATE MACHINES (FSM)

A. Moore Machines

B. Mealy Machines

REFERENCES

- [1] Wiktionary contributors. circuit. Wiktionary, the free dictionary. [Online]. Available: <https://en.wiktionary.org/wiki/circuit>
- [2] ——. digital. Wiktionary, the free dictionary. [Online]. Available: <https://en.wiktionary.org/wiki/digital>